

Maciej Byczko Bartosz Matysiak	Prowadzący: dr inż. Jacek Mazurkiewicz	Numer ćwiczenia 5
PN 10:50 TP	Temat ćwiczenia: Układy Kombinacyjne i Sekwencyjne w VHDL-u	Ocena:
Grupa: B	Data wykonania: 6 Grudnia 2021r.	

Spis treści

1	Zadanie 1	3
1.1	Polecenie	3
1.2	Rozwiązanie	3
1.2.1	Tabela prawdy	3
1.2.2	Siatka Karnaugh	4
1.3	Zapis za pomocą równań boolowskich	4
1.3.1	Kod VHDL	4
1.4	Kod VHDL TestBench	4
1.4.1	Symulacja	6
1.4.2	Fizyczna implementacja (Kod UCF)	6
1.5	Zapis tablicowy	6
1.5.1	Kod VHDL	6
1.6	Kod VHDL TestBench	6
1.6.1	Symulacja	8
1.6.2	Fizyczna implementacja (Kod UCF)	8
2	Zadanie 2	8
2.1	Polecenie	8
2.2	Rozwiązanie	9
2.2.1	Tabela prawdy	9
2.2.2	Siatki Karnaugh	9
2.3	Zapis za pomocą równań boolowskich	10
2.3.1	Kod VHDL	10
2.4	Kod VHDL TestBench	10
2.4.1	Symulacja	12
2.4.2	Fizyczna implementacja (Kod UCF)	12
2.5	Zapis tablicowy	12
2.5.1	Kod VHDL	12
2.6	Kod VHDL TestBench	13
2.6.1	Symulacja	14
2.6.2	Fizyczna implementacja (Kod UCF)	14
3	Zadanie 3	15
3.1	Polecenie	15
3.2	Rozwiązanie	15
3.2.1	Opis symboliki	15
3.2.2	Schemat grafowy	16
3.2.3	Tabela prawdy	16
3.2.4	Kod VHDL	17
3.2.5	Kod VHDL TestBench	18
3.2.6	Symulacja	20

3.2.7	Fizyczna implementacja (Kod UCF)	20
3.3	Implementacja wyświetlacza LED	20
3.3.1	Kod VHDL	20
3.3.2	Kod VHDL TestBench	22
3.3.3	Symulacja	24
3.3.4	Fizyczna implementacja (Kod UCF)	24
4	Zadanie 4	25
4.1	Polecenie	25
4.2	Rozwiązanie	25
4.2.1	Schemat stanów	25
4.2.2	Tabela prawdy	26
4.2.3	Kod VHDL	26
4.2.4	Kod VHDL Testbench	27
4.2.5	Symulacja	28
4.2.6	Fizyczna implementacja (Kod UCF)	28
5	Wnioski	28

1 Zadanie 1

1.1 Polecenie

Implementacja funkcji logicznej $G(w, x, y, z) = \prod(0, 2, 3, 4, 6, 7, 9, 11, 12, 13, 15)$ w VHDL-u za pomocą:

1. Zapis równań boolowskich
2. Metoda zapisu tablicowego

1.2 Rozwiązanie

1.2.1 Tabela prawdy

Kod dziesiętny	w	x	y	z	G
0	0	0	0	0	0
1	0	0	0	1	1
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	1
9	1	0	0	1	0
10	1	0	1	0	1
11	1	0	1	1	0
12	1	1	0	0	0
13	1	1	0	1	0
14	1	1	1	0	1
15	1	1	1	1	0

1.2.2 Siatka Karnaugh

		<i>wx</i>			
		00	01	11	10
<i>yz</i>	00	0	0	0	1
	01	1	1	0	0
	11	0	0	0	0
	10	0	0	1	1

Rysunek 1: $W_{y_j G} = w\bar{x}\bar{z} + \bar{w}yz + wy\bar{z}$

1.3 Zapis za pomocą równań boolowskich

1.3.1 Kod VHDL

```

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity gfunction is
5     Port ( W : in  STD_LOGIC;
6           X : in  STD_LOGIC;
7           Y : in  STD_LOGIC;
8           Z : in  STD_LOGIC;
9           S : out STD_LOGIC);
10 end gfunction;
11
12 architecture Dataflow of gfunction is
13
14 begin
15     S <= (not Z and W and not X) or (not Y and Z and not W) or (Y and
16         not Z and W);
17 end Dataflow;

```

1.4 Kod VHDL TestBench

```

1 LIBRARY ieee;
2 USE ieee.std_logic_1164.ALL;
3
4 ENTITY gfunctionTestbench IS
5 END gfunctionTestbench;
6
7 ARCHITECTURE behavior OF gfunctionTestbench IS


```

```
8
9    — Component Declaration for the Unit Under Test (UUT)
10    COMPONENT gfunction
11    PORT(
12        W : IN    std_logic;
13        X : IN    std_logic;
14        Y : IN    std_logic;
15        Z : IN    std_logic;
16        S : OUT   std_logic
17    );
18    END COMPONENT;
19
20    —Inputs
21    signal W : std_logic := '0';
22    signal X : std_logic := '0';
23    signal Y : std_logic := '0';
24    signal Z : std_logic := '0';
25
26    —Outputs
27    signal S : std_logic;
28 BEGIN
29
30    — Instantiate the Unit Under Test (UUT)
31    uut: gfunction PORT MAP (
32        W => W,
33        X => X,
34        Y => Y,
35        Z => Z,
36        S => S
37    );
38    — Stimulus process
39    stim_procw: process
40    begin
41        wait for 200 ns;
42        w <= not w;
43    end process;
44
45    stim_procx: process
46    begin
47        wait for 100 ns;
48        x <= not x;
49    end process;
50
51    stim_procy: process
52    begin
53        wait for 50 ns;
54        y <= not y;
55    end process;
56
57    stim_procz: process
58    begin
```

```

59     wait for 25 ns;
60     z <= not z;
61     end process;
62
63 END;
```

1.4.1 Symulacja

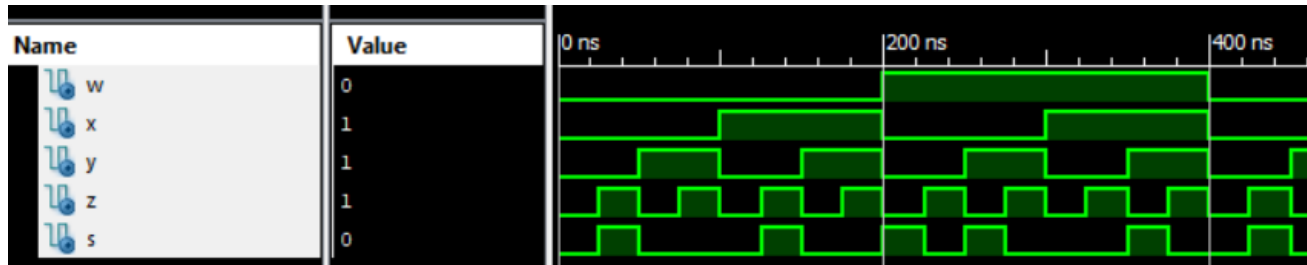

1.4.2 Fizyczna implementacja (Kod UCF)

```

1 # Keys
2 NET "W" LOC = "P42";
3 NET "X" LOC = "P40";
4 NET "Y" LOC = "P43";
5 NET "Z" LOC = "P38";
6
7 # LEDS
8 NET "S" LOC = "P35";
```

1.5 Zapis tablicowy

1.5.1 Kod VHDL

```

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity gfunctiontruthtable is
5     Port ( WEJ : in  STD_LOGIC_VECTOR (3 downto 0);
6           WYJ : out STD_LOGIC);
7 end gfunctiontruthtable;
8
9 architecture Dataflow of gfunctiontruthtable is
10
11 begin
12     with WEJ select
13     WYJ <= '1' when "0001" | "0101" | "1000" | "1010" | "1110",
14           '0' when others;
15 end Dataflow;
```


1.6 Kod VHDL TestBench

```

1 LIBRARY ieee;
2 USE ieee.std_logic_1164.ALL;
3
4 ENTITY gFunctionTestBenchViaTruthTable IS
```

```
5 END gFunctionTestBenchViaTruthTable;
6
7 ARCHITECTURE behavior OF gFunctionTestBenchViaTruthTable IS
8
9     — Component Declaration for the Unit Under Test (UUT)
10    COMPONENT gfunctiontruthtable
11    PORT(
12        WEJ : IN  std_logic_vector(3 downto 0);
13        WYJ : OUT std_logic
14    );
15    END COMPONENT;
16
17    —Inputs
18    signal WEJ : std_logic_vector(3 downto 0) := (others => '0');
19
20    —Outputs
21    signal WYJ : std_logic;
22 BEGIN
23
24    — Instantiate the Unit Under Test (UUT)
25    uut: gfunctiontruthtable PORT MAP (
26        WEJ => WEJ,
27        WYJ => WYJ
28    );
29
30    — Stimulus process
31    stim_proc0: process
32    begin
33        wait for 25 ns;
34        WEJ(0) <= not WEJ(0);
35    end process;
36
37    stim_proc1: process
38    begin
39        wait for 50 ns;
40        WEJ(1) <= not WEJ(1);
41    end process;
42
43    stim_proc2: process
44    begin
45        wait for 100 ns;
46        WEJ(2) <= not WEJ(2);
47    end process;
48
49    stim_proc3: process
50    begin
51        wait for 200 ns;
52        WEJ(3) <= not WEJ(3);
53    end process;
54 END;
```

1.6.1 Symulacja

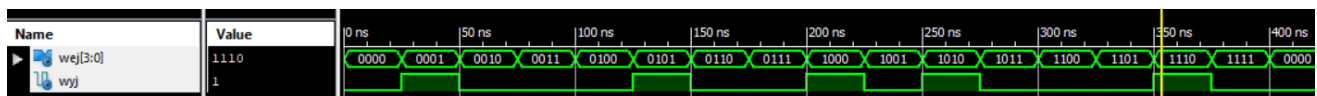

1.6.2 Fizyczna implementacja (Kod UCF)

```

1 # Keys
2 NET "WEJ(0)" LOC = "P42";
3 NET "WEJ(1)" LOC = "P40";
4 NET "WEJ(2)" LOC = "P43";
5 NET "WEJ(3)" LOC = "P38";
6
7 # Leds
8 NET "WYJ" LOC = "P35";

```

2 Zadanie 2

2.1 Polecenie

Implementacja układu translatora kodu **4-bit kod NKB na 4-bit kod Aikena** w VHDL-u za pomocą:

1. Zapis równań boolowskich
2. Metoda zapisu tablicowego

2.2 Rozwiązanie

2.2.1 Tabela prawdy

Kod dziesiętny	NKB				Kod Aikena			
	w	x	y	z	w	x	y	z
0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	1
2	0	0	1	0	0	0	1	0
3	0	0	1	1	0	0	1	1
4	0	1	0	0	0	1	0	0
5	0	1	0	1	1	0	1	1
6	0	1	1	0	1	1	0	0
7	0	1	1	1	1	1	0	1
8	1	0	0	0	1	1	1	0
9	1	0	0	1	1	1	1	1
10	1	0	1	0	-	-	-	-
11	1	0	1	1	-	-	-	-
12	1	1	0	0	-	-	-	-
13	1	1	0	1	-	-	-	-
14	1	1	1	0	-	-	-	-
15	1	1	1	1	-	-	-	-

2.2.2 Siatki Karnaugh

		<i>yz</i>			
		00	01	11	10
<i>wx</i>	00	0	0	0	0
	01	0	1	1	1
	11	-	-	-	-
	10	1	1	-	-

$w_A = xz + xy + w$

		<i>yz</i>			
		00	01	11	10
<i>wx</i>	00	0	0	0	0
	01	1	0	1	1
	11	-	-	-	-
	10	1	1	-	-

$x_A = x\bar{z} + xy + w$

		<i>yz</i>			
		00	01	11	10
<i>wx</i>	00	0	0	1	1
	01	0	1	0	0
	11	-	-	-	-
	10	1	1	-	-

$$y_A = \bar{x}y + x\bar{y}z + w$$

		<i>yz</i>			
		00	01	11	10
<i>wx</i>	00	0	1	1	0
	01	0	1	1	0
	11	-	-	-	-
	10	0	1	-	-

$$z_A = z$$

2.3 Zapis za pomocą równań boolowskich

2.3.1 Kod VHDL

```

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity boolean_aiken is
5     Port ( w : in  STD_LOGIC;
6           x : in  STD_LOGIC;
7           y : in  STD_LOGIC;
8           z : in  STD_LOGIC;
9           a : out STD_LOGIC;
10          b : out STD_LOGIC;
11          c : out STD_LOGIC;
12          d : out STD_LOGIC);
13 end boolean_aiken;
14
15 architecture Dataflow of boolean_aiken is
16
17 begin
18 a <= (x and z) or (x and y) or (w);
19 b <= (x and not z) or (x and y) or (w);
20 c <= (not x and y) or (x and not y and z) or (w);
21 d <= (z);
22
23 end Dataflow;

```

2.4 Kod VHDL TestBench

```

1 LIBRARY ieee;
2 USE ieee.std_logic_1164.ALL;
3
4 ENTITY boolean_aiken_testbench IS
5 END boolean_aiken_testbench;
6
7 ARCHITECTURE behavior OF boolean_aiken_testbench IS

```

```

8
9      — Component Declaration for the Unit Under Test (UUT)
10     COMPONENT boolean_aiken
11     PORT(
12         w : IN    std_logic;
13         x : IN    std_logic;
14         y : IN    std_logic;
15         z : IN    std_logic;
16         a : OUT   std_logic;
17         b : OUT   std_logic;
18         c : OUT   std_logic;
19         d : OUT   std_logic
20     );
21     END COMPONENT;
22
23     —Inputs
24     signal w : std_logic := '0';
25     signal x : std_logic := '0';
26     signal y : std_logic := '0';
27     signal z : std_logic := '0';
28
29     —Outputs
30     signal a : std_logic;
31     signal b : std_logic;
32     signal c : std_logic;
33     signal d : std_logic;
34 BEGIN
35
36     — Instantiate the Unit Under Test (UUT)
37     uut: boolean_aiken PORT MAP (
38         w => w,
39         x => x,
40         y => y,
41         z => z,
42         a => a,
43         b => b,
44         c => c,
45         d => d
46     );
47
48     — Stimulus process
49     stim_procw: process
50     begin
51         wait for 200 ns;
52         w <= not w;
53     end process;
54
55     stim_procx: process
56     begin
57         wait for 100 ns;
58         x <= not x;


```

```

59     end process ;
60
61     stim_procy: process
62     begin
63         wait for 50 ns ;
64         y <= not y ;
65     end process ;
66
67     stim_procz: process
68     begin
69         wait for 25 ns ;
70         z <= not z ;
71     end process ;
72 END;

```

2.4.1 Symulacja

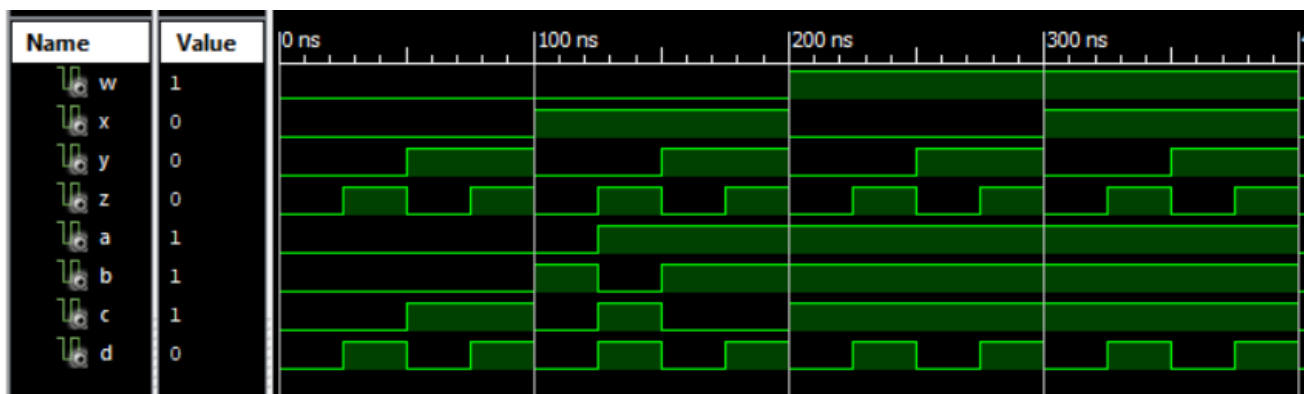

2.4.2 Fizyczna implementacja (Kod UCF)

```

1 # Keys
2 NET "Z" LOC = "P42";
3 NET "Y" LOC = "P40";
4 NET "X" LOC = "P43";
5 NET "W" LOC = "P38";
6
7 # LEDS
8 NET "D" LOC = "P35";
9 NET "C" LOC = "P29";
10 NET "B" LOC = "P33";
11 NET "A" LOC = "P34";

```

2.5 Zapis tablicowy

2.5.1 Kod VHDL

```

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity table_aiken is
5     Port ( WEJ : in  STD_LOGIC_VECTOR (3 downto 0);
6           A : out  STD_LOGIC;

```

```

7         B : out  STD_LOGIC;
8         C : out  STD_LOGIC;
9         D : out  STD_LOGIC);
10 end table_aiken;
11
12 architecture Dataflow of table_aiken is
13
14 begin
15 with WEJ select
16   A <= '0' when "0000" | "0001" | "0010" | "0011" | "0100",
17       '1' when others;
18 with WEJ select
19   B <= '0' when "0000" | "0001" | "0010" | "0011" | "0101",
20       '1' when others;
21 with WEJ select
22   C <= '0' when "0000" | "0001" | "0100" | "0110" | "0111",
23       '1' when others;
24 with WEJ select
25   D <= '0' when "0000" | "0010" | "0100" | "0110" | "1000",
26       '1' when others;
27
28 end Dataflow;

```

2.6 Kod VHDL TestBench

```


1 LIBRARY ieee;
2 USE ieee.std_logic_1164.ALL;
3
4 ENTITY table_aiken_testbench IS
5 END table_aiken_testbench;
6
7 ARCHITECTURE behavior OF table_aiken_testbench IS
8
9     — Component Declaration for the Unit Under Test (UUT)
10    COMPONENT table_aiken
11    PORT(
12        WEJ : IN  std_logic_vector(3 downto 0);
13        A : OUT  std_logic;
14        B : OUT  std_logic;
15        C : OUT  std_logic;
16        D : OUT  std_logic
17    );
18    END COMPONENT;
19
20
21    —Inputs
22    signal WEJ : std_logic_vector(3 downto 0) := (others => '0');
23
24    —Outputs
25    signal A : std_logic;
26    signal B : std_logic;
27    signal C : std_logic;

```

```

28     signal D : std_logic;
29
30 BEGIN
31
32     — Instantiate the Unit Under Test (UUT)
33     uut: table_aiken PORT MAP (
34         WEJ => WEJ,
35         A => A,
36         B => B,
37         C => C,
38         D => D
39     );
40
41     — Stimulus process
42     stim_proc0: process
43     begin
44         wait for 25 ns;
45         WEJ(0) <= not WEJ(0);
46     end process;
47
48     stim_proc1: process
49     begin
50         wait for 50 ns;
51         WEJ(1) <= not WEJ(1);
52     end process;
53
54     stim_proc2: process
55     begin
56         wait for 100 ns;
57         WEJ(2) <= not WEJ(2);
58     end process;
59
60     stim_proc3: process
61     begin
62         wait for 200 ns;
63         WEJ(3) <= not WEJ(3);
64     end process;
65
66 END;
```

2.6.1 Symulacja

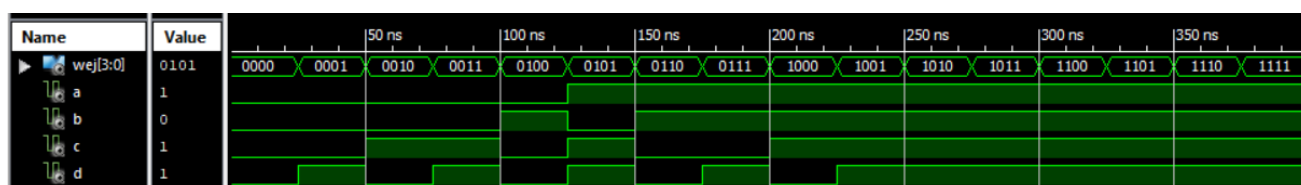

2.6.2 Fizyczna implementacja (Kod UCF)

```

1 # Keys
2 NET "WEJ(0)" LOC = "P42";
```

```
3 NET "WEJ(1)" LOC = "P40";
4 NET "WEJ(2)" LOC = "P43";
5 NET "WEJ(3)" LOC = "P38";
6
7 # LEDS
8 NET "D" LOC = "P35";
9 NET "C" LOC = "P29";
10 NET "B" LOC = "P33";
11 NET "A" LOC = "P34";
```

3 Zadanie 3

3.1 Polecenie

Detektor sekwencji 11011, automat Mealy-ego, jedno wejście, jedno wyjście, brak resetu, sekwencja prawidłowa 5-bitowa w VHDL-u jako maszyna stanów.

3.2 Rozwiązanie

3.2.1 Opis symboliki

Alfabet wejściowy

- $z_0 = 0$
- $z_1 = 1$


Stany wewnętrzne

- q_0 - stan początkowy | wprowadzono niepoprawny ciąg bitów
- q_1 - wprowadzono pierwszą cyfrę prawidłowego ciągu
- q_2 - wprowadzono drugą cyfrę prawidłowego ciągu
- q_3 - wprowadzono trzecią cyfrę prawidłowego ciągu
- q_4 - wprowadzono czwartą cyfrę prawidłowego ciągu
- q_5 - wprowadzono poprawną sekwencję

Alfabet wyjścia

- y_0 - Wprowadzony ciąg nadal jest niepoprawny
- y_1 - Wprowadzono poprawną sekwencję

3.2.2 Schemat grafowy

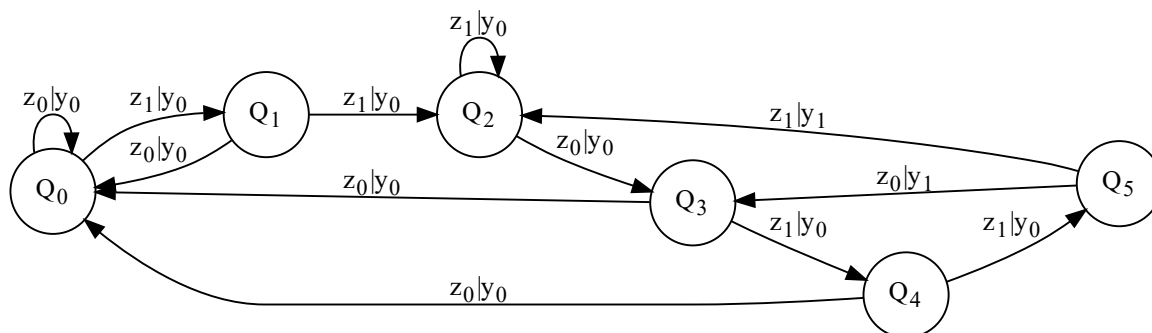

3.2.3 Tabela prawdy

S	Q(t)			Z	Q(t+1)			Y
	Q_2	Q_1	Q_0		Q_2	Q_1	Q_0	
Q_0	0	0	0	0	0	0	0	0
Q_0	0	0	0	1	0	0	1	0
Q_1	0	0	1	0	0	0	0	0
Q_1	0	0	1	1	0	1	0	0
Q_2	0	1	0	0	0	1	1	0
Q_2	0	1	0	1	0	1	0	0
Q_3	0	1	1	0	0	0	0	0
Q_3	0	1	1	1	1	0	0	0
Q_4	1	0	0	0	0	0	0	0
Q_4	1	0	0	1	1	0	1	0
Q_5	1	0	1	0	0	1	1	1
Q_5	1	0	1	1	0	1	0	1
-	1	1	0	0	-	-	-	-
-	1	1	0	1	-	-	-	-
-	1	1	1	0	-	-	-	-
-	1	1	1	1	-	-	-	-

3.2.4 Kod VHDL

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity detectormodule is
5     Port ( Z : in  STD_LOGIC;
6           CLK : in  STD_LOGIC;
7           Y : out STD_LOGIC);
8 end detectormodule;
9
10 architecture Behavioral of detectormodule is
11
12 type state_type is (Q0, Q1, Q2, Q3, Q4, Q5);
13 signal state: state_type := Q0;
14 signal next_state : state_type := Q0;
15
16 begin
17     process1 : process(CLK)
18     begin
19         if rising_edge(CLK) then
20             state <= next_state;
21         end if;
22     end process process1;
23
24     process2: process(state , Z)
25     begin
26         next_state <= state; — default
27         case state is
28             when Q0 =>
29                 if Z = '1' then
30                     next_state <= Q1;
31                 end if;
32             when Q1 =>
33                 if Z = '0' then
34                     next_state <= Q0;
35                 else
36                     next_state <= Q2;
37                 end if;
38             when Q2 =>
39                 if Z = '0' then
40                     next_state <= Q3;
41                 end if;
42             when Q3 =>
43                 if Z = '0' then
44                     next_state <= Q0;
45                 else
46                     next_state <= Q4;
47                 end if;
48             when Q4 =>
49                 if Z = '0' then
```

```

50     next_state <= Q0;
51     else
52         next_state <= Q5;
53     end if;
54 when Q5 =>
55     if Z = '0' then
56         next_state <= Q3;
57     else
58         next_state <= Q2;
59     end if;
60 end case;
61 end process process2;
62
63 — process3
64 Y <= '1' when state = Q5 else '0'; — brak rozniczy miedzy
    automatem moorea i mealyego
65
66 end Behavioral;

```

3.2.5 Kod VHDL TestBench

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3
4  ENTITY detectorTestBench IS
5  END detectorTestBench;
6
7  ARCHITECTURE behavior OF detectorTestBench IS
8
9      — Component Declaration for the Unit Under Test (UUT)
10     COMPONENT detectormodule
11     PORT(
12         Z : IN  std_logic;
13         CLK : IN  std_logic;
14         Y : OUT  std_logic
15     );
16     END COMPONENT;
17
18     —Inputs
19     signal Z : std_logic := '0';
20     signal CLK : std_logic := '0';
21
22     —Outputs
23     signal Y : std_logic;
24
25     — Clock period definitions
26     constant CLK_period : time := 100 ns;
27
28 BEGIN
29
30     — Instantiate the Unit Under Test (UUT)
31     uut: detectormodule PORT MAP (


```

```
32         Z => Z,
33         CLK => CLK,
34         Y => Y
35     );
36
37     — Clock process definitions
38     CLK_process : process
39     begin
40         CLK <= '0';
41         wait for CLK_period/2;
42         CLK <= '1';
43         wait for CLK_period/2;
44     end process;
45
46     — Stimulus process
47     stim_proc: process
48     begin
49         — initial : '0'
50         wait for 125 ns;
51
52         Z <= '1';
53         wait for 100 ns;
54
55         Z <= '0';
56         wait for 100 ns;
57
58         Z <= '1';
59         wait for 300 ns;
60
61         Z <= '0';
62         wait for 200 ns;
63
64         Z <= '1';
65         wait for 200 ns;
66
67         Z <= '0';
68         wait for 100 ns;
69
70         Z <= '1';
71         wait for 100 ns;
72
73         Z <= '0';
74         wait for 100 ns;
75
76         Z <= '1';
77         wait for 200 ns;
78
79         Z <= '0';
80         wait for 100 ns;
81
82
```

```

83     Z <= '1';
84     wait for 200 ns;
85
86     Z <= '0';
87     wait for 100 ns;
88
89     Z <= '1';
90     wait for 100 ns;
91 end process;
92
93 END;
```

3.2.6 Symulacja

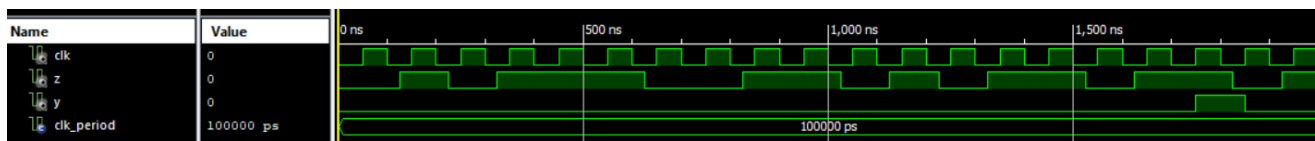

3.2.7 Fizyczna implementacja (Kod UCF)

```

1 # Clocks
2 NET "CLK" LOC = "P7" | BUFG = CLK | PERIOD = 5ms HIGH 50%;
3
4 # Keys
5 NET "Z" LOC = "P42";
6
7 # LEDs
8 NET "Y" LOC = "P35";
```

3.3 Implementacja wyświetlacza LED

3.3.1 Kod VHDL

```

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity detector_led is
5     Port ( Z : in  STD_LOGIC;
6           Y : out STD_LOGIC;
7           LED : out STD_LOGIC_VECTOR (7 downto 0);
8           CLK : in  STD_LOGIC);
9 end detector_led;
10
11 architecture Behavioral of detector_led is
12
13 type state_type is (Q0, Q1, Q2, Q3, Q4, Q5);
14 signal state: state_type := Q0;
15 signal next_state : state_type := Q0;
16
17 begin
18
19 process_clk : process(CLK)
```

```
20  begin
21      if rising_edge(CLK) then
22          state <= next_state;
23      end if;
24  end process process_clk;
25
26  process2: process(state, Z)
27  begin
28      next_state <= state; — default
29      case state is
30          when Q0 =>
31              if Z = '1' then
32                  next_state <= Q1;
33              end if;
34          when Q1 =>
35              if Z = '0' then
36                  next_state <= Q0;
37              else
38                  next_state <= Q2;
39              end if;
40          when Q2 =>
41              if Z = '0' then
42                  next_state <= Q3;
43              end if;
44          when Q3 =>
45              if Z = '0' then
46                  next_state <= Q0;
47              else
48                  next_state <= Q4;
49              end if;
50          when Q4 =>
51              if Z = '0' then
52                  next_state <= Q0;
53              else
54                  next_state <= Q5;
55              end if;
56          when Q5 =>
57              if Z = '0' then
58                  next_state <= Q3;
59              else
60                  next_state <= Q2;
61              end if;
62      end case;
63  end process process2;
64
65  — process3
66  Y <= '1' when state = Q5 else '0'; — brak roznicy miedzy
67      automatem moorea i mealyego
68
69  process3: process(state)
70  begin
```

```

70         case state is
71         when Q5 =>
72             LED <= "10010010";
73         when Q4 =>
74             LED <= "10011001";
75         when Q3 =>
76             LED <= "10110000";
77         when Q2 =>
78             LED <= "10100100";
79         when Q1 =>
80             LED <= "11111001";
81         when Q0 =>
82             LED <= "11000000";
83         end case;
84     end process process3;
85
86
87 end Behavioral;

```

3.3.2 Kod VHDL TestBench

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3
4  ENTITY detector_led_testbench IS
5  END detector_led_testbench;
6
7  ARCHITECTURE behavior OF detector_led_testbench IS
8
9      — Component Declaration for the Unit Under Test (UUT)
10
11     COMPONENT detector_led
12     PORT(
13         Z : IN  std_logic;
14         Y : OUT std_logic;
15         LED : OUT std_logic_vector(7 downto 0);
16         CLK : IN  std_logic
17     );
18     END COMPONENT;
19
20
21     —Inputs
22     signal Z : std_logic := '0';
23     signal CLK : std_logic := '0';
24
25     —Outputs
26     signal Y : std_logic;
27     signal LED : std_logic_vector(7 downto 0);
28
29     — Clock period definitions
30     constant CLK_period : time := 100 ns;
31

```


```
32 BEGIN
33
34 — Instantiate the Unit Under Test (UUT)
35 uut: detector_led PORT MAP (
36     Z => Z,
37     Y => Y,
38     LED => LED,
39     CLK => CLK
40 );
41
42 — Clock process definitions
43 CLK_process : process
44 begin
45     CLK <= '0';
46     wait for CLK_period/2;
47     CLK <= '1';
48     wait for CLK_period/2;
49 end process;
50
51
52
53 — Stimulus process
54 stim_proc: process
55 begin
56     — initial : '0'
57     wait for 125 ns;
58
59     Z <= '1';
60     wait for 100 ns;
61
62     Z <= '0';
63     wait for 100 ns;
64
65     Z <= '1';
66     wait for 300 ns;
67
68     Z <= '0';
69     wait for 200 ns;
70
71     Z <= '1';
72     wait for 200 ns;
73
74     Z <= '0';
75     wait for 100 ns;
76
77     Z <= '1';
78     wait for 100 ns;
79
80     Z <= '0';
81     wait for 100 ns;
82
```

```

83     Z <= '1';
84     wait for 200 ns;
85
86     Z <= '0';
87     wait for 100 ns;
88
89     Z <= '1';
90     wait for 200 ns;
91
92     Z <= '0';
93     wait for 100 ns;
94
95     Z <= '1';
96     wait for 100 ns;
97 end process;
98
99 END;

```

3.3.3 Symulacja

 

3.3.4 Fizyczna implementacja (Kod UCF)

```

1 # Clocks
2 NET "CLK" LOC = "P7" | BUFG = CLK | PERIOD = 5ms HIGH 50%;
3
4 # Keys
5 NET "Z" LOC = "P42";
6
7 # LEDS
8 NET "Y" LOC = "P35";
9
10 # DISPL. 7-SEG
11 NET "LED(0)" LOC = "P12"; # Seg. A; shared with LED<10>
12 NET "LED(1)" LOC = "P13"; # Seg. B; shared with LED<8>
13 NET "LED(2)" LOC = "P22"; # Seg. C; shared with LED<12>
14 NET "LED(3)" LOC = "P19"; # Seg. D; shared with LED<14>
15 NET "LED(4)" LOC = "P14"; # Seg. E; shared with LED<15>
16 NET "LED(5)" LOC = "P11"; # Seg. F; shared with LED<9>
17 NET "LED(6)" LOC = "P20"; # Seg. G; shared with LED<13>
18 NET "LED(7)" LOC = "P18"; # Seg. DP; shared with LED<11>

```

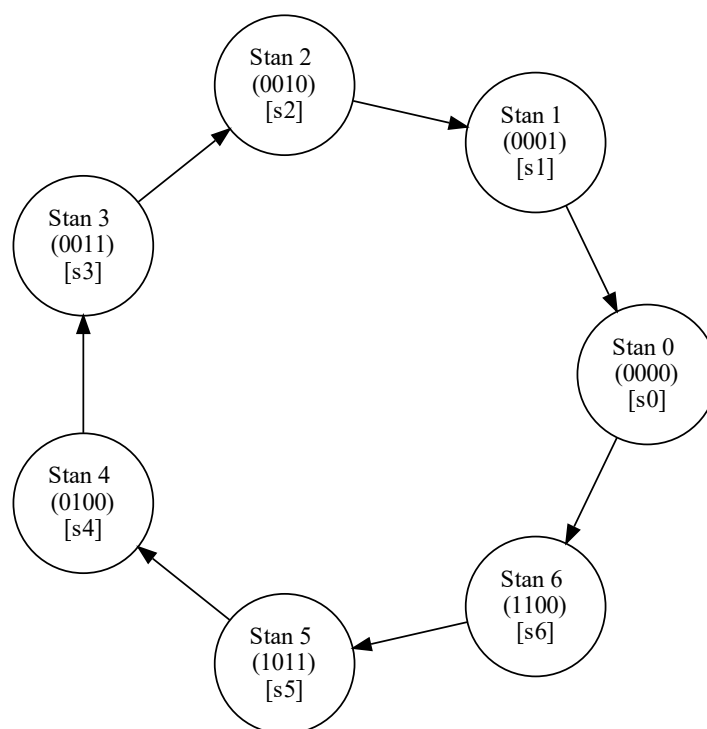

4 Zadanie 4

4.1 Polecenie

Zaprojektować licznik synchroniczny liczący w tył na bazie kodu Aikena w zakresie 0-6 (mod 7) jako maszyna stanów.

4.2 Rozwiązanie

4.2.1 Schemat stanów



4.2.2 Tabela prawdy

n	Q(t)				Q(t+1)			
	Q_3	Q_2	Q_1	Q_0	Q_3	Q_2	Q_1	Q_0
0	0	0	0	0	1	1	0	0
1	0	0	0	1	0	0	0	0
2	0	0	1	0	0	0	0	1
3	0	0	1	1	0	0	1	0
4	0	1	0	0	0	0	1	1
5	1	0	1	1	0	1	0	0
6	1	1	0	0	1	0	1	1

4.2.3 Kod VHDL

```

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity aiken_counter is
5     Port ( CLK : in  STD_LOGIC;
6           Q : out  STD_LOGIC_VECTOR (3 downto 0));
7 end aiken_counter;
8
9 architecture Behavioral of aiken_counter is
10
11     type state_type is (s6, s5, s4, s3, s2, s1, s0);
12     signal state : state_type := s6;
13
14 begin
15
16     processc: process(CLK)
17     begin
18         if rising_edge(CLK) then
19             case state is
20                 when s6 => state <= s5 after 5ns;
21                 when s5 => state <= s4 after 5ns;
22                 when s4 => state <= s3 after 5ns;
23                 when s3 => state <= s2 after 5ns;
24                 when s2 => state <= s1 after 5ns;
25                 when s1 => state <= s0 after 5ns;
26                 when s0 => state <= s6 after 5ns;

```

```

27     end case;
28   end if;
29 end process processc;
30
31 Q(3) <= '1' when state = s6 or state = s5 else '0';
32 Q(2) <= '1' when state = s6 or state = s4 else '0';
33 Q(1) <= '1' when state = s5 or state = s3 or state = s2 else '0';
34 Q(0) <= '1' when state = s5 or state = s3 or state = s1 else '0';
35
36 end Behavioral;

```

4.2.4 Kod VHDL Testbench

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.ALL;
3
4  ENTITY aiken_counter_testbench IS
5  END aiken_counter_testbench;
6
7  ARCHITECTURE behavior OF aiken_counter_testbench IS
8
9      — Component Declaration for the Unit Under Test (UUT)
10     COMPONENT aiken_counter
11     PORT(
12         CLK : IN    std_logic;
13         Q : OUT    std_logic_vector(3 downto 0)
14     );
15     END COMPONENT;
16
17     —Inputs
18     signal CLK : std_logic := '0';
19
20     —Outputs
21     signal Q : std_logic_vector(3 downto 0);
22
23     — Clock period definitions
24     constant CLK_period : time := 10 ns;
25
26 BEGIN
27
28     — Instantiate the Unit Under Test (UUT)
29     uut: aiken_counter PORT MAP (
30         CLK => CLK,
31         Q => Q
32     );
33
34     — Clock process definitions
35     CLK_process : process
36     begin
37         CLK <= '0';
38         wait for CLK_period/2;
39         CLK <= '1';


```

```

40     wait for CLK_period/2;
41     end process;
42 END;

```

4.2.5 Symulacja

 

4.2.6 Fizyczna implementacja (Kod UCF)

```

1 # Clocks
2 NET "CLK" LOC = "P7" | BUFG = CLK | PERIOD = 5ms HIGH 50%;
3
4 # LEDS
5 NET "Q(0)" LOC = "P35";
6 NET "Q(1)" LOC = "P29";
7 NET "Q(2)" LOC = "P33";
8 NET "Q(3)" LOC = "P34";

```

5 Wnioski

Na początku trudność sprawiło nam testowanie modułów w języku VHDL. Problem rozwiązał się sam, w momencie, gdy natknęliśmy się na materiał instruktażowy, w którym pokazane zostało, że przy testowaniu modułu, plik testowy vhd należy wygenerować na podstawie napisanego modułu (sam moduł nie stanowi pliku testowego).

Zadanie 3 wymagało od nas podłączenia wyświetlacza LED, mieliśmy dostępny już gotowy moduł lecz wymagał on od nas narysowania schematu co jest bardzo żmudne. Obeszliśmy to poprzez własną implementację wyjść aby wyświetlić odpowiednie cyfry na wyświetlaczu.

Wszystkie zadania zostały wykonane bardzo sprawnie i bez większych problemów, tworzenie układów w kodzie VHDL jest znacznie przyjemniejsze niż rysowanie schematów ponieważ jest szybsze i łatwiejsze w szukaniu błędów gdyż edytor sam nam powie, z którą linijką jest coś nie tak.